Microprocessors & Interfacing

Input/Output Devices

Lecturer: Annie Guo

COMP9032 Week8

Lecture Overview

- · Input devices
 - Input switches
 - Keypads
- · Output devices
 - LCD

COMP9032 Week8

Input Switches

- · Most basic binary input devices
- · A switch provides different values, depending on the switch position.
- · Pull-up resistor/circuit is necessary in each switch to provide a high logic level when the switch is open.
- · Problem with switches:
 - Switch bounce.
 - When a switch makes contact, its mechanical springiness will cause the contact to bounce, namely contact and break, for a few milliseconds (typically 5 to 10 ms).

COMP9032 Week8

Input Switches (cont.) Vcc Vcc Logic high with switch open Logic low with switch closed 741 S244 Data Bus Octal Buffer (a) Single-pole, single-throw (SPST) logic switch (b) Multiple pole switch COMP9032 Week8

NAND Latch Debouncer Logic high with switch up Logic low with switch down COMP9032 Week8

Software Debouncing

- · Basic idea: wait until the switch is stable
- For example:
 - Wait and see:
 - If the software detects a low logic level, indicating that switch has closed, it simply waits for some time, say 20 to 100ms, and then test if the switch is still low.
 - Counter-based approach:
 - · Initialize a counter to 10.
 - · Poll the switch every millisecond until the counter is either 0 or
 - If the switch output is low, decrease the counter; otherwise,
 - increment the counter.


 If the counter is 0, we know that switch output has been low (closed) for at least 10 ms. If, on the other hand, the counter reaches 20, we know that the switch output has been high for at least 10 ms

COMP9032 Week8

One-Dimensional Array of Switches (cont.)

- · Switch bouncing problem must be solved
 - Either using software or hardware
- The array of switches must be scanned to find out which switches are closed or open.
 - Software is required to scan the array. As the software outputs a 3-bit sequence from 000 to 111, the multiplexer selects each of the switch inputs.
 - The output of switch array can be interfaced directly to an eight-bit port at point A.

COMP9032 Week8

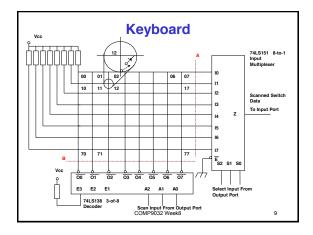

Keyboard (cont.)

- A keyboard is an array of switches arranged in a two-dimensional matrix.
- A switch is connected at each intersection of the vertical and horizontal lines.
- Closing the switch connects the horizontal line to the vertical line.
- 8*8 keyboard can be interfaced directly to 8bit output and input ports at point A and B

COMP9032 Week8

Keyboard (cont.)

- Software can scan the key board by selecting each column line via a decoder and then scanning each row via a multiplexer to find the closed switch or switches.
 - The combination of the two 3-bit scan codes (A2A1A0 and S2S1S0) identifies which switch is closed. For example, the code 001 010 scan switch 12, as highlighted.
 - When a switch is scanned, it will output a logic 0 if it is closed.
- · The diode prevents a problem called ghosting.

COMP9032 Week8

Ghosting*

R3 R2 R1 Col 0 Col 1 Col 2


R0w 0 (Pulled low, error)
Row 1 (Pulled low, OK)
Row 2 (High, OK)


Low
(Scanned column)

Ghosting (cont.)*


- Ghosting occurs when several keys are pushed at once.
- Consider the case shown in the figure in the previous slide, where three switches 01, 10 and 11 are all closed. Column 0 is selected with a logic low and assume that the circuit does not contain the diodes.
 As the rows are scanned, a low is sensed on Row 1, which is true because switch 10 is closed. But, a low is also seen on Row 0, indicating switch 00 is closed, which is NOT true.
- The diodes in the switches eliminate this problem by preventing current flow from R1 through switches 01 and 11. Thus Row 0 will not be low when it is scanned.


COMP9032 Week8

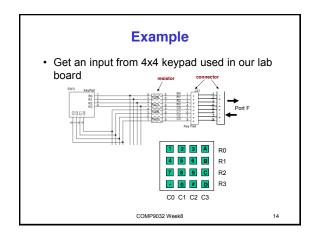


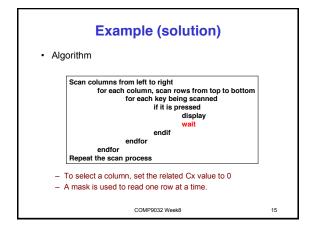


Code Implementation ; The program gets input from keypad and displays its ascii value on the .include "m2560def.inc" .def row = r16 ; current row number .def col = r17 ; current column number .def rmask = r18 : mask for current row during scan .def cmask = r19 ; mask for current column during scan .def temp1 = r20 .def temp2 = r21 ; PF7-4: output, PF3-0, input .equ PORTFDIR = 0xF0 .egu INITCOLMASK = 0xEF : scan from the leftmost column. .equ INITROWMASK = 0x01 ; scan from the top row egu ROWMASK =0x0F ; for obtaining input from Port F COMP9032 Week8

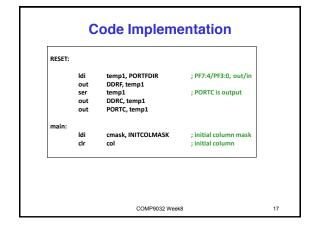


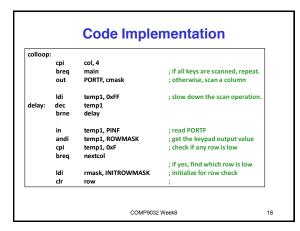

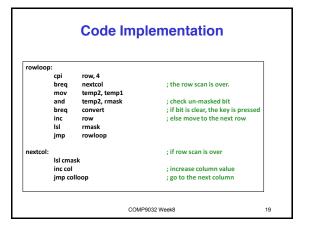


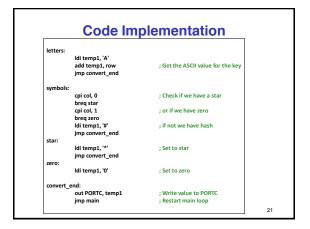Code Implementation convert: ; If the pressed key is in col. 3 col, 3 breq letters ; we have a letter ; If the key is not in col. 3 and row, 3 ; if the key is in row3, breq ; we have a symbol or 0 temp1, row ; Otherwise we have a number in 1-9 mov temp1, row ; temp1 = row*3 + col temp1, col temp1, -'1' subi ; Add the value of character '1' convert_end COMP9032 Week8 20



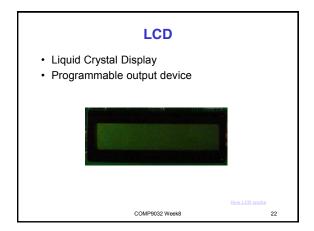

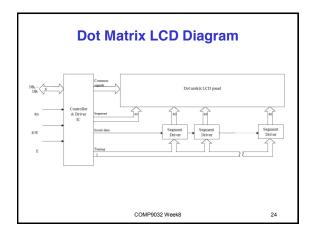Characters are displayed using a dot matrix. 5x7, 5x8, and 5x11 A controller is used for communication between the LCD and other components, e.g. MCU The controller has an internal character generator ROM. All display functions are controllable by instructions.



Pin Number	Symbol	
1	V_{ss}	
2	V_{cc}	
3	V_{ee}	
4	RS	
5	R/W	
6	E	
7	DB0	
8	DB1	
9	DB2	
10	DB3	
11	DB4	
12	DB5	
13	DB6	
14	DB7	1

| Proceedings | Procedings | Pr

Operations

- MCU communicates with LCD through two registers
 - Instruction Register (IR)
 - To store instruction code like Display Clear or Cursor Shift as well as addresses for the Display Data RAM (DD RAM) or the Character Generator RAM (CG RAM)
 - Data Register (DR)
 - To temporarily store data to be read/written to/from the DD RAM of the display controller.

COMP9032 Week8

...

Operations (cont.)

 The register select (RS) signal determines which of these two registers is selected.

RS	R/W	Operation
0	0	IR write, internal operation (Display Clear etc.)
0	1	Busy flag (DB ₇) and Address Counter (DB ₀ ~ DB ₆) read
1	0	DR Write, Internal Operation (DR ~ DD RAM or CG RAM)
1	1	DR Read, Internal Operation (DD RAM or CG RAM)

COMP9032 Week8

Operations (cont.)

- When the busy flag is high or "1", the LCD module is busy with the internal operation.
- The next instruction must not be written until the busy flag is low or "0".
- For details, refer to the LCD USER'S MANUAL.

COMP9032 Week8

29

LCD Instructions

- A list of binary instructions are available for LCD operations
- Some typical ones are explained in the next slides.

COMP9032 Week8

30

Instructions

Clear Display

RS R/W DB7 DB6 DB5 BD4 DB3 DB2 DB1 DB0 Code 0 0 0 0 0 0 0 0 0 1

- The display clears and the cursor or blink moves to the upper left corner of the display.
- The execution of the clear display instruction sets entry mode to increment mode.

COMP9032 Week8

Instructions

· Return Home

RS R/W DB7 DB6 DB5 BD4 DB3 DB2 DB1 DB0 Code 0 0 0 0 0 0 0 1

- The cursor or the blink moves to the upper left corner of the display. Text on the display remains unchanged.

COMP9032 Week8

Instructions

· Entry Mode Set

RS R/W DB7 DB6 DB5 BD4 DB3 DB2 DB1 DB0 Code 0 0 0 0 0 0 1 I/D

- Set the Increment/Decrement and Shift modes to the desired settings.
 - I/D: Increments (I/D = 1) or decrements (I/D = 0) the DD RAM address by 1 when a character code is written into or read from the DD RAM.
 - The cursor or blink moves to the right when incremented by 1.
 - · The same applies to writing and reading the CG RAM.
 - · S: Shifts the entire display either to the right or to the left when S = 1; shift to the left when I/D = 1 and to the right when I/D = 0.

COMP9032 Week8

Instructions

Display ON/OFF Control

RS R/W DB7 DB6 DB5 BD4 DB3 DB2 DB1 DB0 Code 0 0 0 0 0 1 D C B

- Control the display ON/OFF status, Cursor ON/OFF and Cursor Blink function.
 - D: The display is ON when D = 1 and OFF when D = 0.
 - C: The cursor displays when C = 1 and does not display when C = 0.
 - B: The character indicated by the cursor blinks when B =

COMP9032 Week8

Instructions

· Cursor or Display Shift

RS R/W DB7 DB6 DB5 BD4 DB3 DB2 DB1 DB0 Code 0 0 0 0 1 S/C R/L x x

- Shift the cursor position or display to the right or left without writing or reading display data.

S/C R/L

- O Shifts cursor position to the left (AC is decremented by one)

 Shifts cursor position to the right (AC is 1) 0
- Shifts cursor position to the right (AC is incremented by one)
- Shifts the entire display to the left. The cursor follows the display shift.
- Shifts the entire display to the right. The cursor follows the display shift.

COMP9032 Week8

Instructions

· Function Set

RS R/W DB7 DB6 DB5 BD4 DB3 DB2 DB1 DB0 Code 0 0 0 0 1 DL N F

- Set the interface data length, the number of lines, and character font.
 - DL = "1", 8 -bits; otherwise 4 bits
 - · N: Sets the number of lines
 - N = "0" : 1 line displayN = "1" : 2 line display
 - · F: Sets character font. - F = "1" : 5 x 10 dots
 - F = "0" : 5 x 7 dots

COMP9032 Week8

Instructions

· Read Busy Flag and Address

RS R/W DB7 DB6 DB5 BD4 DB3 DB2 DB1 DB0 Code 0 1 BF A A A A A A

- Read the busy flag (BF) and value of the address counter (AC). BF = 1 indicates that an internal operation is in progress and the next instruction will not be accepted until BF is set to "0". If the display is written while BF = 1, abnormal operation will occur.

COMP9032 Week8


Instructions CG or DD PAM

· Write Data to CG or DD RAM

RS R/W DB7 DB6 DB5 BD4 DB3 DB2 DB1 DB0 Code 1 0 D D D D D D D D

- Write binary 8-bit data DDDDDDDD to the CG or DD RAM.
- The previous designation determines whether the CG or DD RAM is to be written (CG RAM address set or DD RAM address set). After a write the entry mode will automatically increase or decrease the address by 1. Display shift will also follow the entry mode.

COMP9032 Week8

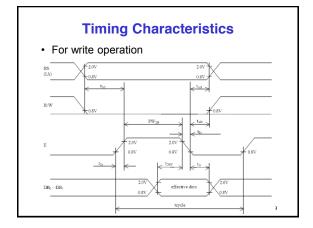

Examples · Send a command to LCD General purpose register data stores value to be written to the LCD Port F is output and connects to LCD; Port A controls the LCD. Assume all labels are pre-defined. macro lcd write com out PORTF, data ; set the data port's value up ldi temp (0<<LCD_RS)|(0<<LCD_RW) ; RS = 0, RW = 0 for a command write ; delay to meet timing (Set up time) out PORTA, temp sbi PORTA, LCD_E ; turn on the enable pin ; delay to meet timing (Enable pulse width) nop cbi PORTA, LCD_E ; turn off the enable pin ; delay to meet timing (Enable cycle time) nop nop nop

Examples · Send data to display ; comments are same as in previous slide. .macro lcd_write_data out PORTF, data : set the data port's value up ldi temp, (1 << LCD_RS)|(0<<LCD_RW) out PORTA, temp ; RS = 1, RW = 0 for a data write ; delay to meet timing (Set up time) sbi PORTA, LCD_E ; turn on the enable pin ; delay to meet timing (Enable pulse width) nop cbi PORTA, LCD_E ; turn off the enable pin ; delay to meet timing (Enable cycle time) nop


Examples · Check LCD and wait until LCD is not busy ; comments are same as in the previous slide .macro lcd_wait_busy clr temp out DDRF, temp ; Make PORTF be an input port for now out PORTF, temp ldi temp, 1 << LCD_RW out PORTA, temp ; RS = 0, RW = 1 for a command port read busy loop: nop sbi PORTA, LCD_E ; delay to meet set-up time ; turn on the enable pin ; delay to meet timing (Data delay time) in temp, PINF cbi PORTA, LCD_E : read value from LCD ; turn off the enable pin ; if the busy flag is set sbrc temp, LCD BI rjmp busy_loop clr temp out PORTA, temp : repeat comma ; else ; turn off read mode, ser temp out DDRF, temp ; make PORTF an output port again


LCD Initialization

- · LCD should be initialized before use
- Internal Reset Circuit can be used, but it is related to power supply loading, may not work properly.
- Therefore, software initialization is recommended.

COMP9032 Week8

,

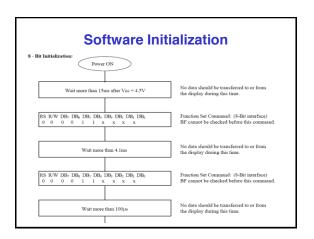

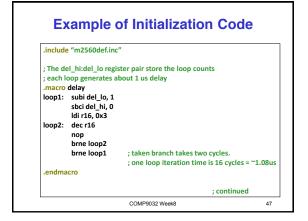

Example of Initialization Code ldi del_lo, low(15000) ;delay (>15ms) ldi del_hi, high(15000) delay ; Function set command with N = 1 and F = 0 ; for 2 line display and 5*7 font. The 1st command ldi data, LCD_FUNC_SET | (1 << LCD_N) lcd_write_com ldi del_lo, low(4100) ; delay (>4.1 ms) ldi del_hi, high(4100) delay lcd_write_com ; 2nd Function set command : continued COMP9032 Week8

Example of Initialization Code ldi del_lo, low(100) ; delay (>100 ns) ldi del_hi, high(100) delav lcd_write_com ; 3rd Function set command lcd_write_com ; Final Function set command lcd_wait_busy ; Wait until the LCD is ready Idi data, LCD_DISP_OFF lcd_write_com ; Turn Display off Icd_wait_busy ; Wait until the LCD is ready Idi data, LCD_DISP_CLR ; Clear Display lcd_write_com ; continued COMP9032 Week8

Example of Initialization Code

COMP9032 Week8

Reading Material

- Chapter 9: Computer Buses and Parallel Input and Output. Microcontrollers and Microcomputers by Fredrick M. Cady.
 - Simple I/O Devices
- · DOT Matrix LCD User's Manual
 - Available on the course website.

COMP9032 Week8

51

Homework

Write an assembly program to initialize LCD panel to display characters in one line with 5x7 font.

COMP9032 Week8